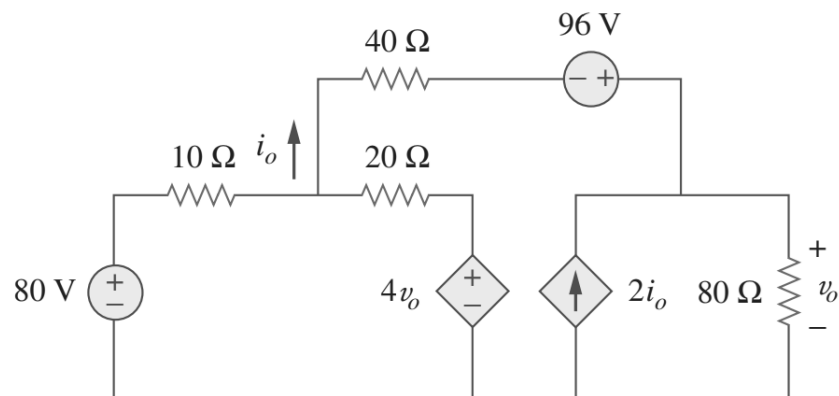


ENGR 065: Circuit Theory

Problem Set #5


Read Chapter 3 from [1] and then solve the following problems.

Problem 1 [25%]: Compute v_o using node-voltage method.




(Hint: test your solution by checking that $i_o = -4.48\text{A}$)

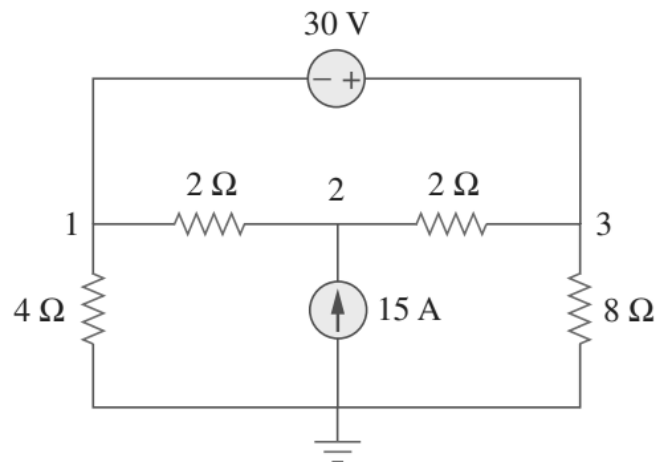Problem 2 [25%] Determine node voltages in the following circuit.




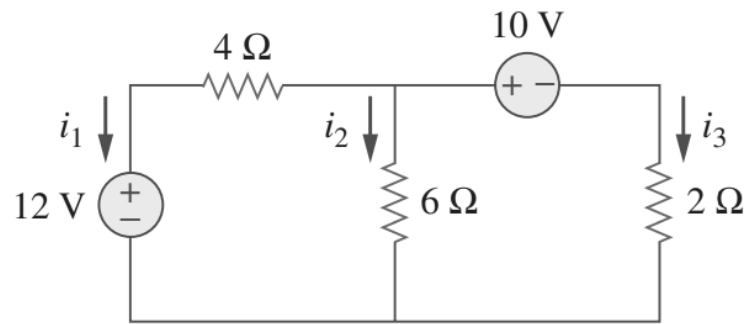Problem 3 [25.5%] Use the mesh-current method to find i_1 , i_2 and i_3 in the following circuit.



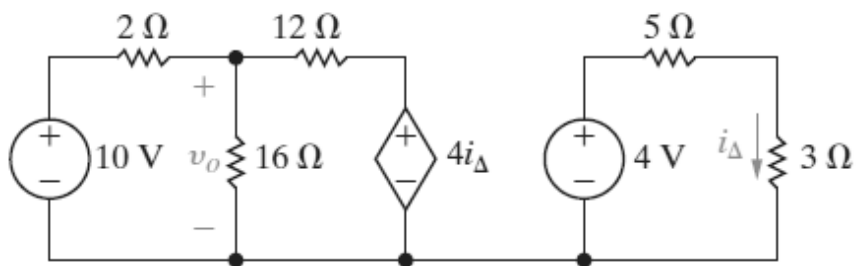Problem 4 [25.5%]

- Use the mesh-current method to find v_o in the following circuit.
- Compute the power delivered by the dependent source.



References

- [1] C. Alexander and M. Sadiku “Fundamentals of Electric Circuits”, 7th Edition, 2021, McGraw-Hill