


ENGR 065: Circuit Theory

Problem Set #2

Read Chapter 2 from [1] and then solve the following problems:

Problem 1 [20%]:

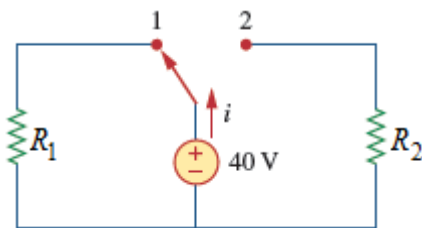- a) Find the resistance of a light bulb rated 40 W, 120 V.
b) Consider the circuit in the given figure. Assume $R_1 = 150\ \Omega$ and $R_2 = 330\ \Omega$.




Calculate current i when the switch is in position 1.


- c) Repeat b) but with switch is in position 2.

Problem 2 [20%]:

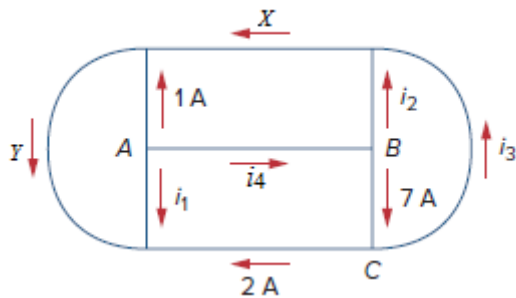- a) Determine i_1 , i_2 , i_3 , and i_4 in the figure below. Consider $X = 4\text{ A}$ and $Y = 5\text{ A}$.



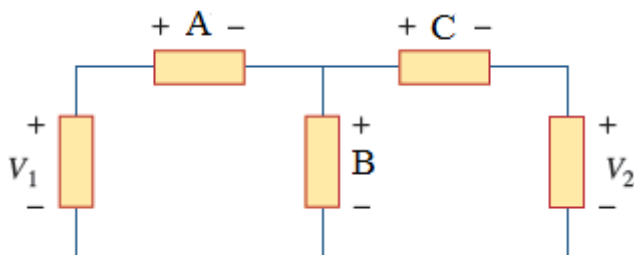- b) In the circuit below, calculate V_1 and V_2 . Assume $A = 19\text{ V}$, $B = 11\text{ V}$, and $C = 10\text{ V}$.




Problem 3 [20%]:


A thermistor is a temperature-sensing element composed of a semiconductor material that exhibits a large change in resistance proportional to a small change in temperature. A particular thermistor has a resistance of $5\text{ k}\Omega$ at 25°C . Its resistance is $340\text{ }\Omega$ at 100°C . Assuming a straight-line relationship between these two values, at what temperature will the thermistor's resistance equal $1\text{ k}\Omega$?

Problem 4 [20%]:

- a) find currents and voltages in the following circuit.
- b) compute the power absorbed/supplied by each element

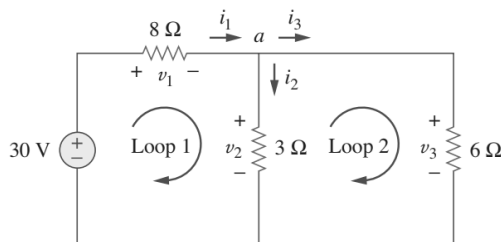**Problem 5 [20%]:**

- a) Find the voltage across each resistor (hint: use KVL)
- b) Find current through each resistor
- c) Find current through each voltage source (hint: use KCL)

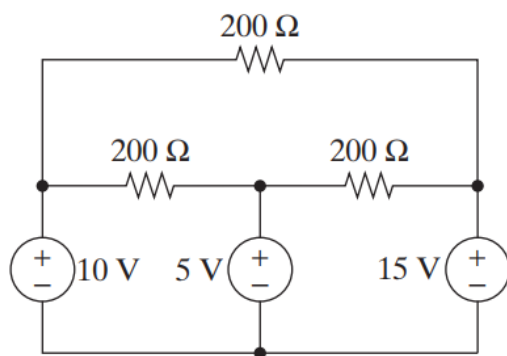**References**

[1] C. Alexander and M. Sadiku “Fundamentals of Electric Circuits”, 7th Edition, 2021, McGraw-Hill