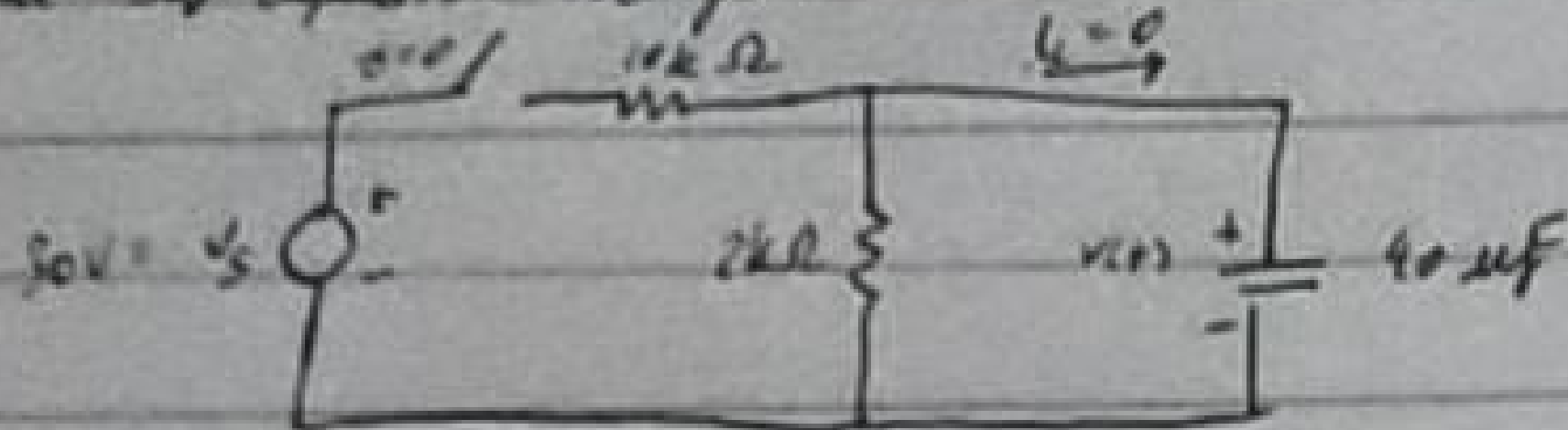


Expt 065

Q.74 Q.5

1. Break at $t=0$ circuit opens. Take $V_s = 30V$

a. find V_c Capacitor Voltage




i. Ideal Circ - Capacitor is open Circ.

$$\therefore V_c(0) = \frac{V_s (2k\Omega)}{10k + 2k} = \frac{60}{12} = 5V$$

b. find $V_c(t)$ for $t > 0$

i. Consider

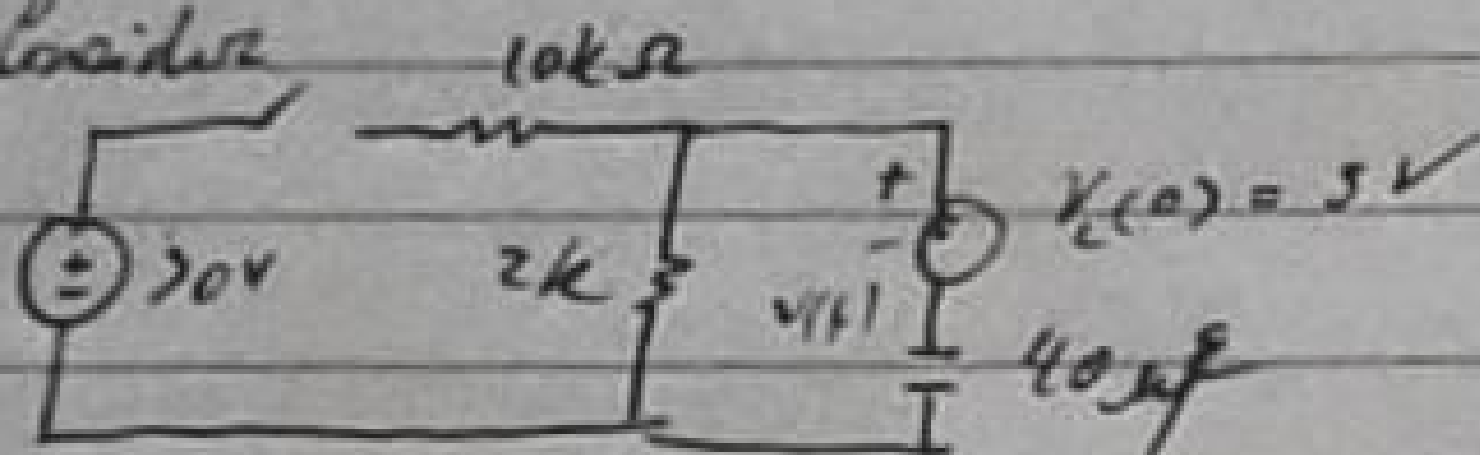

ii. Note that such

circuit complies to the RC condition;

thus, derive exp. form i_0 value.

ii. by refer to $V(t) = V_c(0) e^{-t/\tau}$; $V_c(0) = 5V$; $\tau = RC = 2k \cdot 40\mu F (10^{-6}) = 0.08$

iii. by Thus, $V(t) = 5 e^{-t/0.08}$ ✓


Thus, derive exp. form i_c value.

ii. \hookrightarrow refer to $V(t) = V_c(0) e^{-t/\tau}$; $V_c(0) = 5V$; $\tau = RC = 2k \cdot 10 \mu F (10^{-6}) = 0.02$

iii. \hookrightarrow Thus, $V(t) = 5 e^{-t/0.02}$ ✓


2. Consider switch position move to position b after a long time at $t=0$.

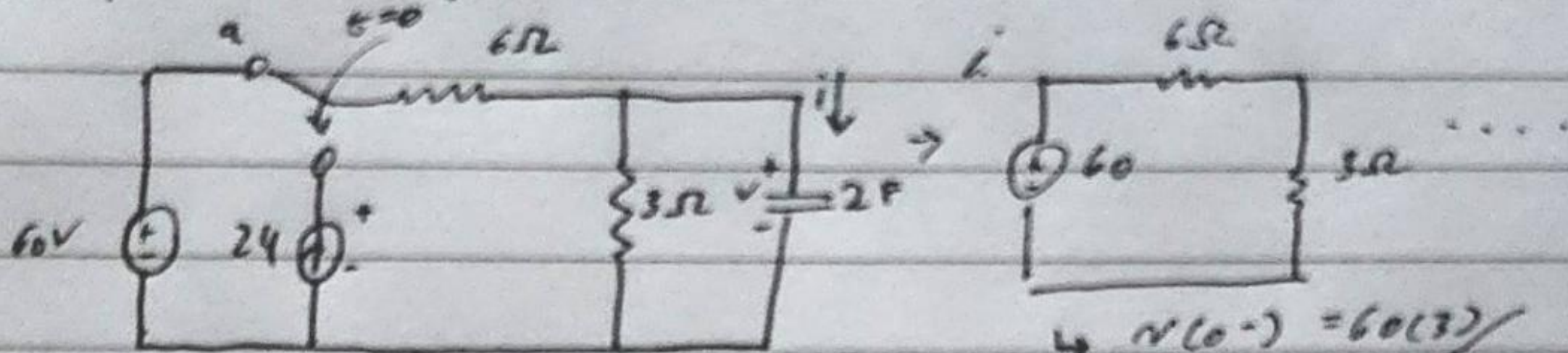a. the capacitor voltage $V(t)$ for $t < 0$ assume DC Cond.



$\hookrightarrow V(0^-) = \frac{60(3)}{6+3} = 20V$; Consider DC Condition
thus, since $V(0^-) = 20$; $V(t) = 20V$ ($V(0^-) = V(0^+)$)

b. at $t=0$ in position b $t > 0$

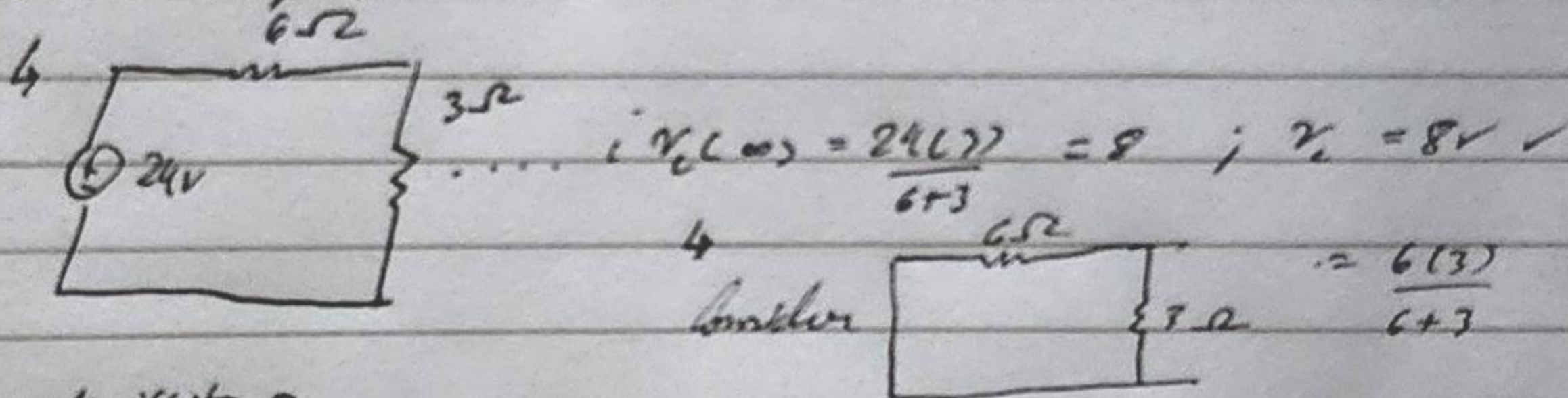

$\hookrightarrow V_c(\infty) = \frac{24(3)}{6+3} = 8$; $V_c = 8V$ ✓

Consider $\tau = \frac{6(3)}{6+3} = 2\Omega$

c. Capacitor current $i(t) > 0$

$\hookrightarrow i(t) = C \frac{dv(t)}{dt} = 2 \frac{d}{dt} (8 + 12 e^{-t/4})$

$\hookrightarrow 2(12) \pi(-\frac{1}{4}) e^{-t/4}$

$\hookrightarrow 6 e^{-t/4} A$ ✓


$\hookrightarrow \tau = Req(C) = 2(2) = 4s$

\hookrightarrow Consider $V(t) = V_c(\infty) + (V_c(0) - V_c(\infty)) e^{-t/\tau}$

$\hookrightarrow 8 + (20 - 8) e^{-t/4}$

$\hookrightarrow V(t) = 8 + 12 e^{-t/4} V$ ✓

3. a. Initial inductor current

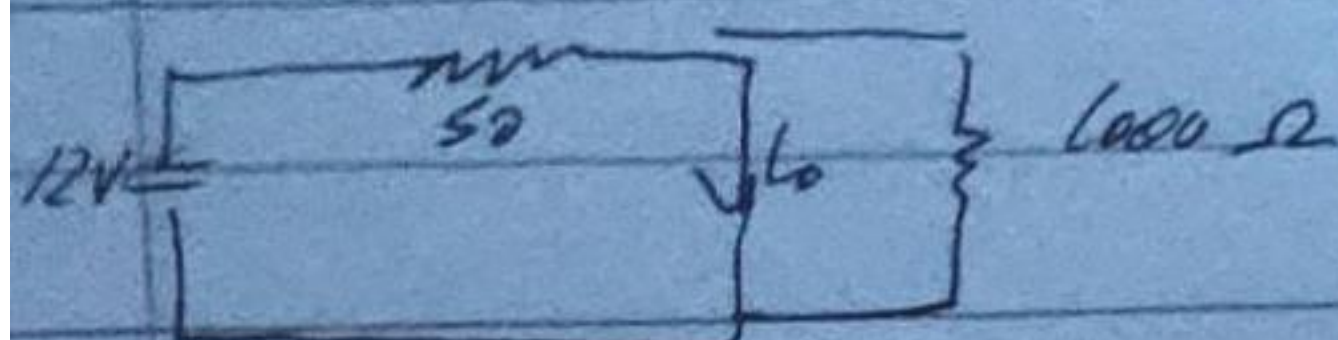

$$\hookrightarrow i_L(0) = \frac{12}{50} = 0.24 \text{ A}$$

b. at $t=0$, switch opens whilst $t \geq 0$

i. $i_L(0) = 0 \text{ A}$ Inductor is shorted

$$\hookrightarrow \tau = \frac{L}{R} = \frac{2}{1000} = 0.002 \text{ s}$$

ii. Consider $i(t) = i(0) + (i(\infty) - i(0))e^{-t/\tau}$; $t = 0.002 \text{ sec}$

$$\hookrightarrow i_L(t) = 0 + (0.24 - 0.24e^{-t/0.002})$$

$$\hookrightarrow i_L(t) = 0.24e^{-500t} \quad \checkmark \quad \checkmark$$

c. Consider $v_o(t) = L \frac{di_L(t)}{dt}$

$$\hookrightarrow v_o(t) = 2(0.24) \frac{d}{dt} e^{-500t}$$

$$\hookrightarrow v_o(t) = -240e^{-500t} \quad \checkmark \quad \checkmark$$

4. Parallel Circuit given capacitor defined as

$$V(t) = 40e^{-1000t} - 90e^{-4000t}, \quad t \geq 0$$

a. Compute the resonance freq (ω_0), zero freq (α), L and R

$$\hookrightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1000 \Rightarrow -2\alpha - 5000 = 2500 \quad \checkmark = \alpha$$

$$s_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -4000 \Rightarrow s - 1000 = -3000 + \sqrt{250000 - \omega_0^2}$$

$$\hookrightarrow \omega_0 = 2000 \text{ rad/sec} \quad \checkmark = \omega_0$$

ii. Consider $Q = \frac{R}{2L} = 2500$

$$\hookrightarrow R = 50 \Omega \quad \checkmark$$

iii. $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\hookrightarrow \frac{1}{\sqrt{10mL}} = 2000$$

$$\hookrightarrow 25 \mu\text{F} \quad \checkmark = C \quad \checkmark$$

b. Compute $i_R(t)$, $i_C(t)$

$$\hookrightarrow \text{small } v(t)/R = i_R(t)$$

$$\hookrightarrow \frac{40e^{-1000t} - 90e^{-4000t}}{50}$$

$$\hookrightarrow \text{small } i_C(t) = C \frac{dv(t)}{dt} = 25 \mu\text{F} \frac{d}{dt} (40e^{-1000t} - 90e^{-4000t})$$

$$\hookrightarrow i_C(t) = (-e^{-1000t} + 9e^{-4000t}) \text{ A}, \quad t \geq 0$$

5. Find Laplace transform of $f(t) = \cos(pt)$

i. Consider $\cos(pt)$

$$f(t) = \frac{1}{2} [e^{ipt} + e^{-ipt}]$$

$$\hookrightarrow x(t) \rightarrow x(s)$$

$$\text{while } e^{s_0 t} x(t) \rightarrow x(s - s_0)$$

$$\hookrightarrow \frac{1}{2} (e^{ipt} + e^{-ipt}) \rightarrow \frac{1}{2} (f(s - ip) + f(s + ip)) \checkmark$$

6. Compute Laplace when $\frac{dv(t)}{dt} + 6v(t) = 9u(t)$; $v(0^-) = -3V$

i. Consider $s v(s) - v(0^-) + 6v(s) = 9/s$; $\frac{dv(t)}{dt} + 6v(t) = 9u(t)$; $v(0^-) = -3V$

$$\hookrightarrow s v(s) + 3 + 6v(s) = 9/s$$

$$\hookrightarrow v(s) (s + 6) = \frac{4}{s} - 3$$

$$\hookrightarrow v(s) = \frac{4 - 3s}{s(s+6)} \checkmark$$

7. Find Laplace transform of

$v(t) = -7ut$ where $u(t)$ is step function

i. Consider $v(t) \rightarrow v(s)$

$$u(t) \rightarrow 1/s$$

$$\text{Then } v(s) = -7/s^2$$

$$v(t) = -7ut \rightarrow -7/s^2 \checkmark$$