

Engg 68 - Circuit Theory

Problem set 10

Use partial expansion to find the time-domain waveform $f(t)$ corresponding to the following transform:

1. as $F(s) = \frac{8}{(s+1)(s+3)}$

$$\therefore \frac{8}{(s+1)(s+3)} = \frac{A}{s+1} + \frac{B}{s+3}$$

$$\hookrightarrow 8 = A(s+3) + B(s+1); \text{ Consider } s = -3, -1$$

$$\text{ii. } s = -3; \hookrightarrow 4(-3+3) + B(-3+1) = 8$$

$$\hookrightarrow -2B = 8 \Rightarrow B = -4 \checkmark$$

$$\text{iii. } s = -1; \hookrightarrow A(-1+3) + B(-1+1) = 8$$

$$\hookrightarrow A(2) + 0 = 8$$

$$\hookrightarrow A = 4 \checkmark$$

iv. Apply Inverse Laplace

$$\mathcal{L}^{-1}\{F(s)\} = \left[\frac{4}{s+1} + \frac{-4}{s+3} \right] \mathcal{L}^{-1}$$

$$\hookrightarrow 4 \mathcal{L}^{-1}\left(\frac{1}{s+1}\right) - 4 \mathcal{L}^{-1}\left(\frac{1}{s+3}\right)$$

$$\hookrightarrow f(t) = 4e^{-t} - 4e^{-3t}$$

$$\hookrightarrow 4(e^{-t} - e^{-3t}) \checkmark$$

$$\text{B } Y(s) = \frac{8}{s(s^2+4s+8)} = 8 \left(\frac{A}{s} + \frac{B}{s^2+2+j^2} + \frac{C}{s^2+2+j^2} \right)$$

$$\text{i. } \hookrightarrow a = \frac{8}{s^2+4s+8}; s=0 = 1$$

$$b = \frac{8}{s(s^2+2+j^2)}; s = -2+j^2 = \frac{8}{s(-2+j^2+2+j^2)} = \frac{8}{s(-j^2)} = \frac{8}{s(1)} = 8$$

$$c = \frac{8}{s(s^2+2+j^2)}; \text{ Consider that } B=C \text{ probably}$$

$$\hookrightarrow c = -0.5 + j0.5$$

$$\text{ii. } Y(s) = \frac{1}{s} + \frac{(0.5+j0.5)}{s+2-j^2} + \frac{(0.5-j0.5)}{s+2+j^2}$$

$$\text{Laplace } \hookrightarrow u(t) + (-0.5+j0.5) \mathcal{L}^{-1}\left(\frac{1}{s+2-j^2}\right) + (-0.5-j0.5) \mathcal{L}^{-1}\left(\frac{1}{s+2+j^2}\right)$$

$$\text{Table } \hookrightarrow u(t) + (-0.5+j0.5)e^{-(2-j^2)t} u(t) + (-0.5-j0.5)e^{-(2+j^2)t} u(t)$$

$$\text{Simplify } \hookrightarrow u(t) + (-0.5+j0.5)e^{-2t}e^{j^2t} u(t) + (-0.5-j0.5)e^{-2t}e^{-j^2t} u(t)$$

$$\text{Distribute } \hookrightarrow u(t) - 0.5e^{-2t}e^{j^2t} u(t) + j0.5e^{-2t}e^{j^2t} u(t) - 0.5e^{-2t}e^{-j^2t} u(t) - j0.5e^{-2t}e^{-j^2t} u(t)$$

$$\text{Associate } \hookrightarrow u(t) - 0.5e^{-2t}(e^{j^2t} + e^{-j^2t}) u(t) + j0.5e^{-2t}(e^{j^2t} - e^{-j^2t}) u(t)$$

$$\hookrightarrow \text{Then, referring to table } \hookrightarrow f(t) = u(t) - e^{-2t} \cos(2t) u(t) - e^{-2t} \sin(2t) u(t)$$

$$c. f(s) = \frac{s}{(s+1)(s+2)^2}$$

$$i. \hookrightarrow f(s) = \frac{A}{s+1} + \frac{B}{s+2} + \frac{C}{(s+2)^2}$$

$$\hookrightarrow s = A(s+2)^2 + B(s+1)(s+2) + C(s+1)$$

$$ii. \hookrightarrow s = -1; A(-1+2)^2 + B(-1+1)(-1+2) + C(-1+1) = 2$$

$$\hookrightarrow s = -2 \Rightarrow C = -2$$

$$iv. \text{ Result. } A = B^* = -2$$

$$\hookrightarrow f(s) = \frac{2}{s+1} - \frac{2}{s+2} - \frac{2}{(s+2)^2}$$

$$v. \hookrightarrow f(x) = 2e^{-t}v(t) - 2e^{-2t}v(t) - 2te^{-2t}v(t) \checkmark$$

Refer to

Laplace

c. Initial and final value of transform

to following transform

$$d) F_1(s) = \frac{100(s+3)}{s(s+5)(s+20)}$$

$$\lim_{s \rightarrow \infty} s \cdot \frac{100(s+3)}{s(s+5)(s+20)}$$

transform $\hookrightarrow \lim_{s \rightarrow \infty} \frac{s(1+\frac{3}{s})100}{s(1+\frac{5}{s})s(1+\frac{20}{s})} = \infty$

property

$$ii. \text{ Consider } \frac{100(0+3)}{(0+5)(0+20)} = \frac{300}{100} = 3 \checkmark$$


$$e. f_2(s) = \frac{s-200}{s(s+50)}$$

$$\hookrightarrow \lim_{s \rightarrow \infty} \frac{s(s-200)}{s(s+50)} = \frac{s-200}{s+50}$$

$$\hookrightarrow \lim_{s \rightarrow \infty} \frac{s(1-\frac{200}{s})}{s(1+\frac{50}{s})} = \frac{1-\frac{200}{\infty}}{1+\frac{50}{\infty}} = 1$$

$$\hookrightarrow \text{Consider } \lim_{s \rightarrow \infty} \frac{s-200}{s+50} = -4 \checkmark$$

Problem 2

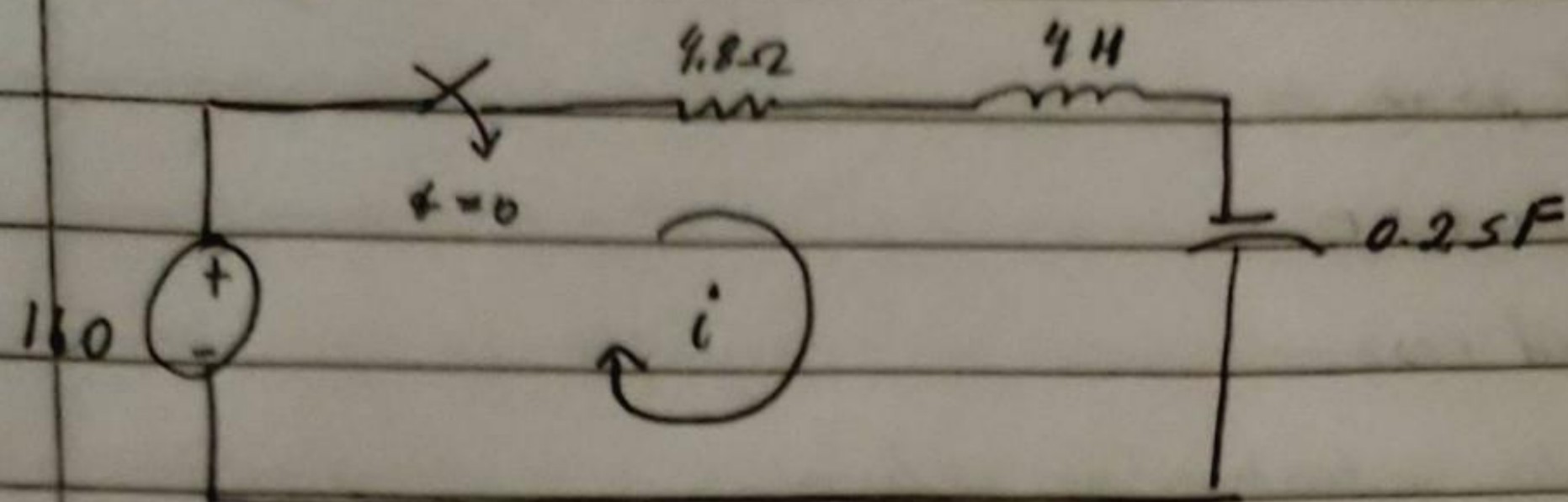

a. The energy stored in the circuit is zero at the time when switch is closed ($t=0$). Find $i(t)$

Laplace • For Circuit Convert Voltage from $v(t) \rightarrow v(s)$ domain
 $v(t) = 160 \Rightarrow v(s) = 160/s$

• Capacitor = $0.25F$ Inductor = $4H$

• Formula $i(s) = \frac{v(s)}{R+Ls+C} = \frac{160/s}{4.8s+4} \checkmark$

b. Compute $i(t)$

i. $i(s) = \frac{160/s}{4.8s+4} = \frac{40/s}{s^2+1.25s+1}$

ii. Consider $s^2+1.25s+1$

$\hookrightarrow s^2+1.25s+0.36+0.64$

$\hookrightarrow (s+0.6)^2+0.64 \Rightarrow (s+0.6)^2+0.8^2$


$\hookrightarrow \frac{50 \cdot 0.8}{(s+0.6)^2+0.8^2} \xleftrightarrow{\text{Eq. 3}} 50 \left[\frac{1}{s+0.6} \cdot \frac{0.8}{(s+0.6)^2+0.8^2} \right]$

• refer to $\frac{\omega_0}{s^2+a^2+\omega_0^2} \xrightarrow{L^{-1}} e^{-at} \sin(\omega_0 t)$

Laplace transform

table

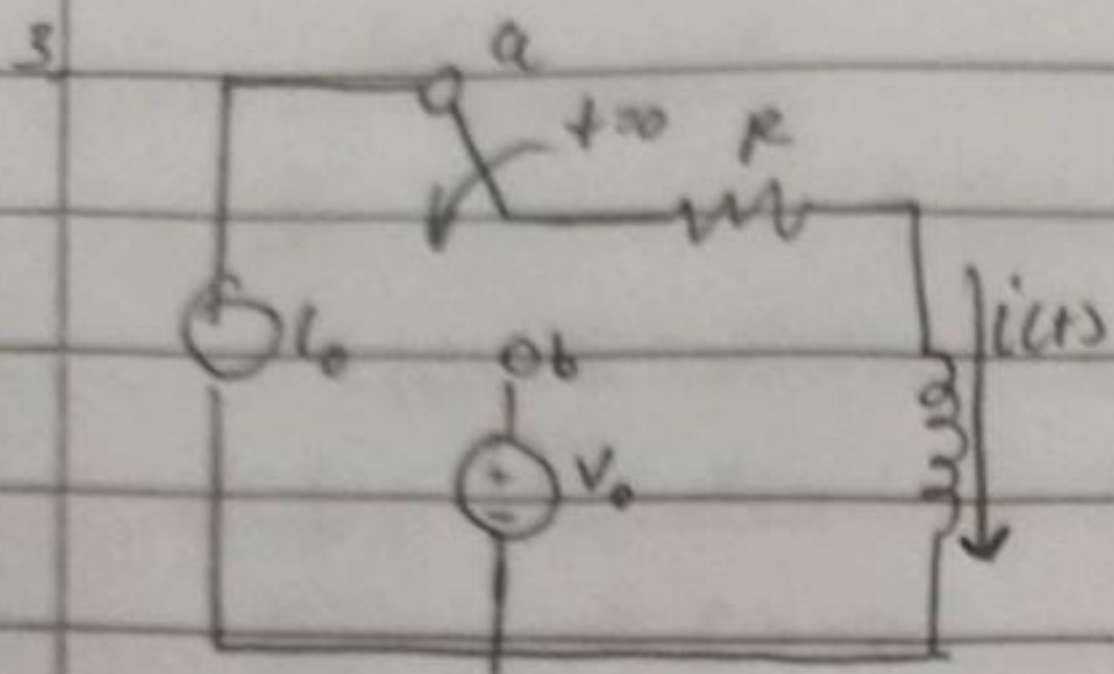iii. \hookrightarrow Therefore, $i(t) = 50e^{-0.6t} \sin(0.8t) \checkmark$




• Switch points to position

be at $t = 0$

so find $i(t)$

• Consider inductor are short

$$i(0) = I_0$$

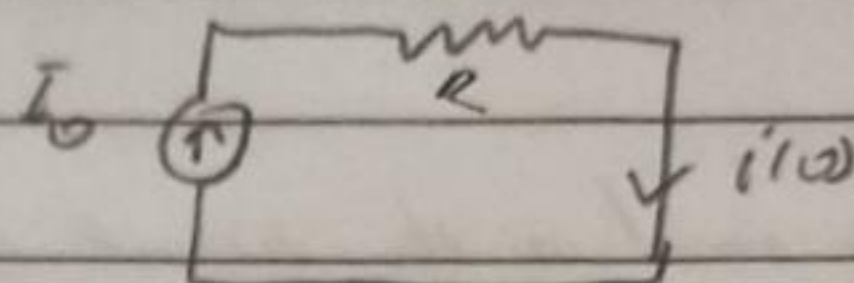

b. Final value theorem of $i(t)$


$$i(\infty) = \lim_{s \rightarrow 0} s I(s) = \lim_{s \rightarrow 0} s \left(\frac{I_0 \cdot L}{s + R/L} + \frac{V_0}{s(s + R/L)} \right)$$

$$\rightarrow \lim_{s \rightarrow 0} \frac{s \cdot I_0}{s + R/L} + \lim_{s \rightarrow 0} \frac{s \cdot V_0}{s(s + R/L)}$$

$$\rightarrow i(\infty) = \frac{0 \cdot I_0}{0 + R/L} + \frac{V_0}{0 + R/L}$$

$$\rightarrow i(\infty) = \frac{V_0}{R} \checkmark$$

\hookrightarrow translate into s-domain

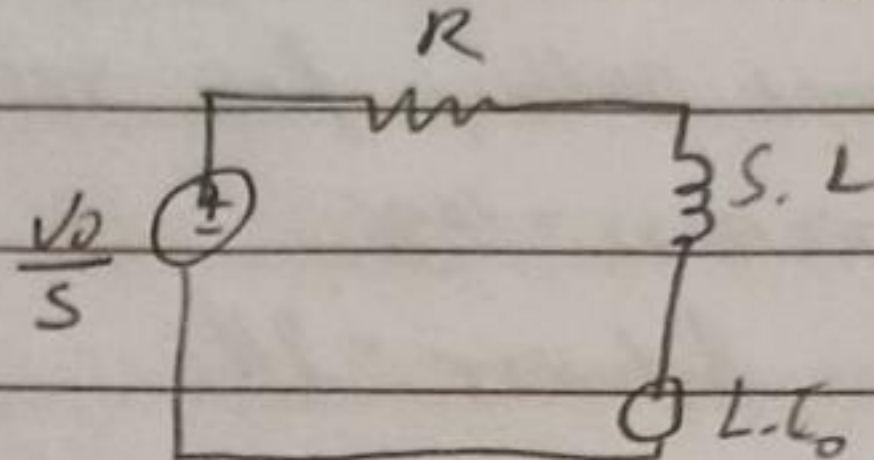

• KVL

$$\rightarrow I(s)(R + sL) = \frac{V_0}{s}$$

$$\rightarrow I(s) = \frac{I_0 \cdot L}{R + sL} + \frac{V_0}{s(R + sL)}$$

• By Partial Fraction

$$\rightarrow I(s) = \frac{I_0 \cdot L}{s + R/L} + \frac{V_0}{s(s + R/L)}$$

$$\rightarrow \frac{V_0}{s(s + R/L)} = \frac{A}{s} + \frac{B}{s + R/L}$$

$$\rightarrow \frac{V_0}{L} = A(s + R/L) + B \cdot s, \quad s = -R/L$$

$$\rightarrow \frac{V_0}{L} = B(-R/L) + 0$$

$$\rightarrow B = -\frac{V_0}{R}$$

$$I(s) = \frac{I_0}{s + R/L} + \frac{V_0}{R} \left(\frac{1}{s} \right) - \frac{V_0}{R} \left(\frac{1}{s + R/L} \right)$$

$$\hookrightarrow I(s) \rightarrow I_0 e^{-t/\tau} + \frac{V_0}{R} - \frac{V_0}{R} e^{-t/\tau} \checkmark$$


c. $\tau = L/R$

by application of
part a

$$\rightarrow i(t) = \left(I_0 - \frac{V_0}{R} \right) e^{-t/\tau} + \frac{V_0}{R} \checkmark$$

4. Find $I_2(s)$ Assume $A = 15 \text{ V}$

• Two initial current in the inductor

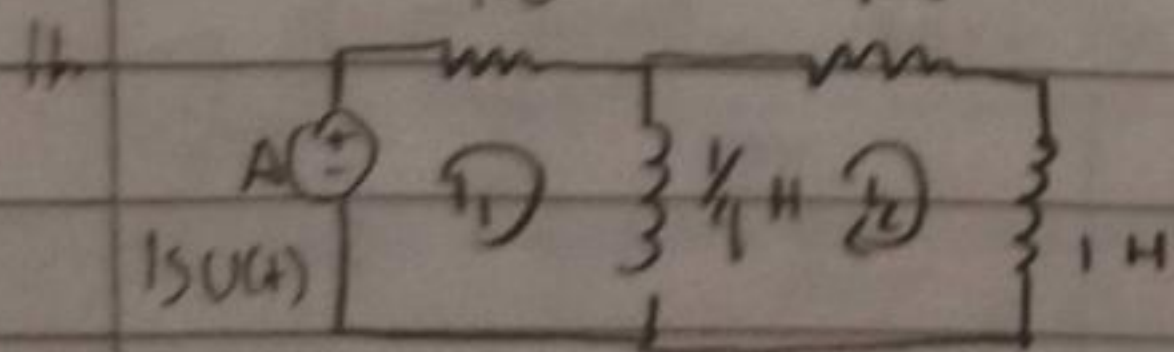

1. Convert Circuit into s-domain


$$\hookrightarrow 15 \text{ V} \rightarrow 15/s$$

$$I_1 \rightarrow I_1(s)$$

$$I_2 \rightarrow I_2(s)$$

$$1/4 \text{ H} \rightarrow 1/4 \cdot s = 0.25s$$
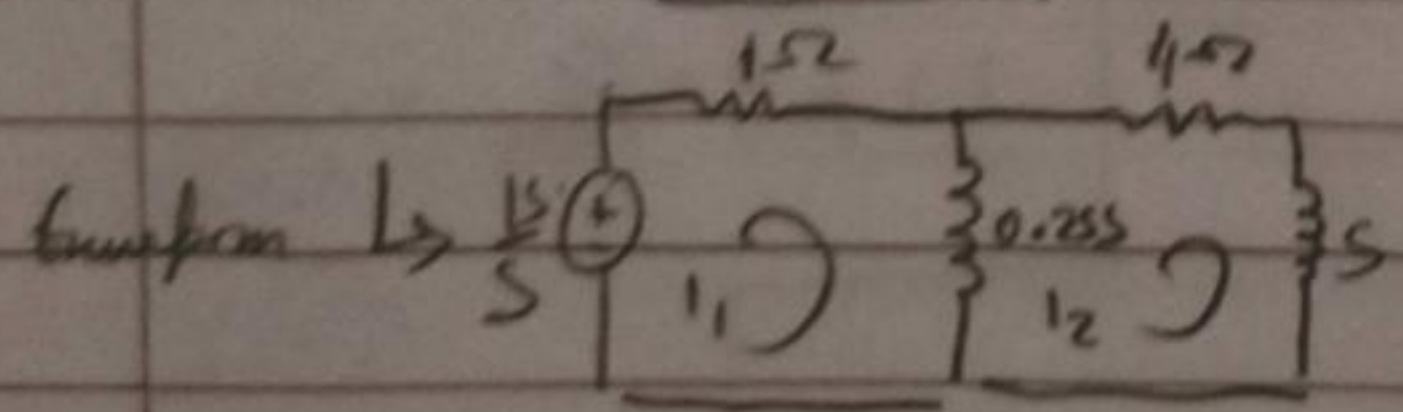
$$1 \text{ H} \rightarrow 1 \cdot s = s$$



$$\text{III. } \bullet \text{ KVL } \rightarrow -\frac{15}{s} + 1(I_1(s) + 0.25s[I_1(s) - I_2(s)]) = 0 \quad \bullet \text{ KVL } I_2$$

$$\rightarrow (1 + 0.25s)I_1(s) - 0.25sI_2(s) = \frac{15}{s}$$

$$\rightarrow 4(I_2(s)) + s \cdot I_2(s) + 0.25s[I_1(s) - I_2(s)] = 0$$

$$\rightarrow (4 + 1.25s)I_2(s) = 0.25sI_1(s)$$


$$\rightarrow \text{Then, } I_1(s) = \frac{(4 + 1.25s)I_2(s)}{0.25s}$$

IV. from Eq 1 & Eq 2

$$\rightarrow (1 + 0.25s) \left(\frac{4 + 1.25s}{0.25s} \right) I_2(s) - 0.25sI_2(s) = \frac{15}{s}$$

$$\rightarrow I_2(s) = \frac{12}{s} + 7.25 + 12.8 \text{ A} \checkmark$$

Problem No. 5

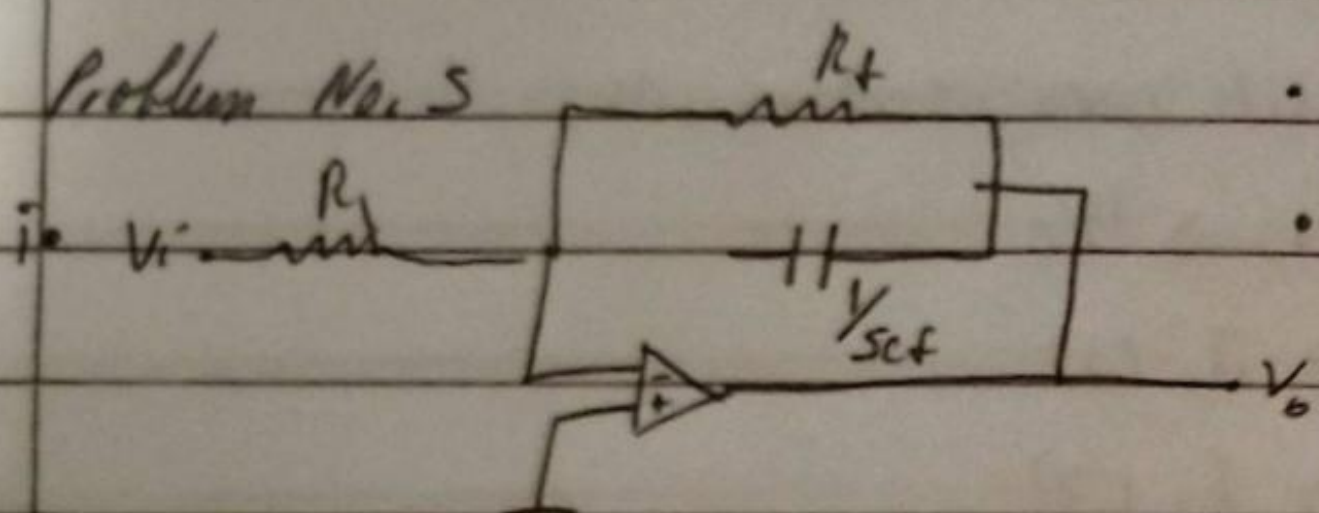


$$\cdot C \Rightarrow \frac{1}{sC}$$

$$\cdot V_+ = V_- = 0V$$

$$\hookrightarrow R_i = \frac{V_i}{i_i}$$

$$\hookrightarrow \text{KVL: } V_o = -i_i \cdot Z_{eq}$$
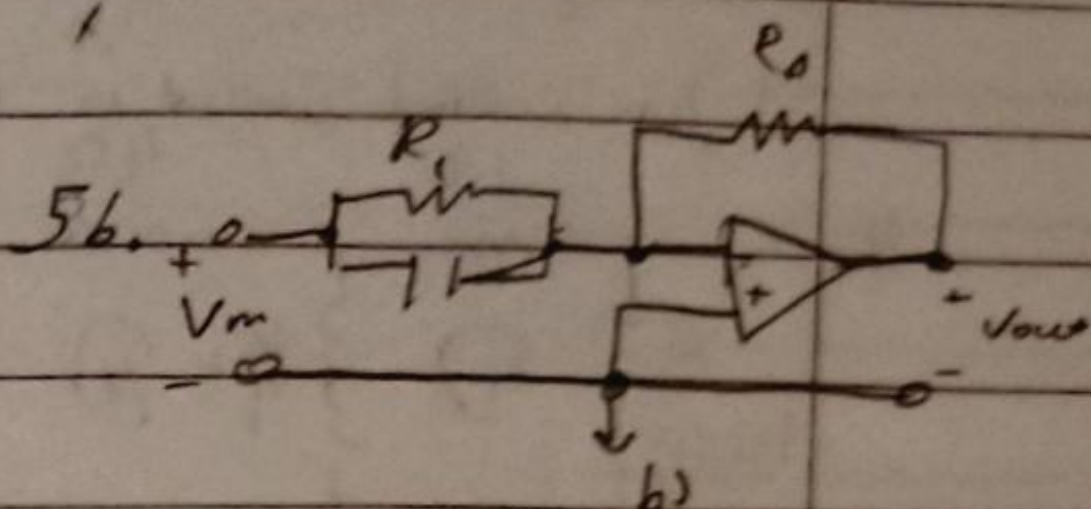
$$V_o = \frac{V_i}{R_i} \times \frac{R_f + \frac{1}{sC}}{R_f + \frac{1}{sC}}; \quad V_o = \frac{-V_i}{R_i} \times \frac{R_f}{1 + sC R_f} \quad \checkmark$$



$$i_i \Rightarrow \rho = \frac{V_i}{Z_{eq}} = \frac{V_i}{R_i + \frac{1}{sC}}$$

$$i_i \hookrightarrow \frac{V_i/R_i}{sR_i C + 1} = \frac{V_i (1 + sC R_i)}{R_i}$$

$$\hookrightarrow V_o = -i_i R_f = \frac{V_i}{R_i} (1 + sC R_i) R_f$$

Thus,

$$V_{out} = -V_i \frac{R_f}{R_i} (1 + sC R_i) \quad \checkmark$$