

Hao Dinh Mui

# Engr 065 - Circuit Theory

## Homework No. 2

7.11.22

1. a) Given a light bulb's rated 40 W and 120 V, what is the resistance?


↳ Consider that Power;  $P = \frac{V^2}{R}$

rearrange to find  $R \rightarrow R = \frac{V^2}{P}$

↳ Thus, considering  $V = (120)^2$   $P = 40 \text{ W}$

$$\rightarrow 1440 / 40 = 360 \Omega$$

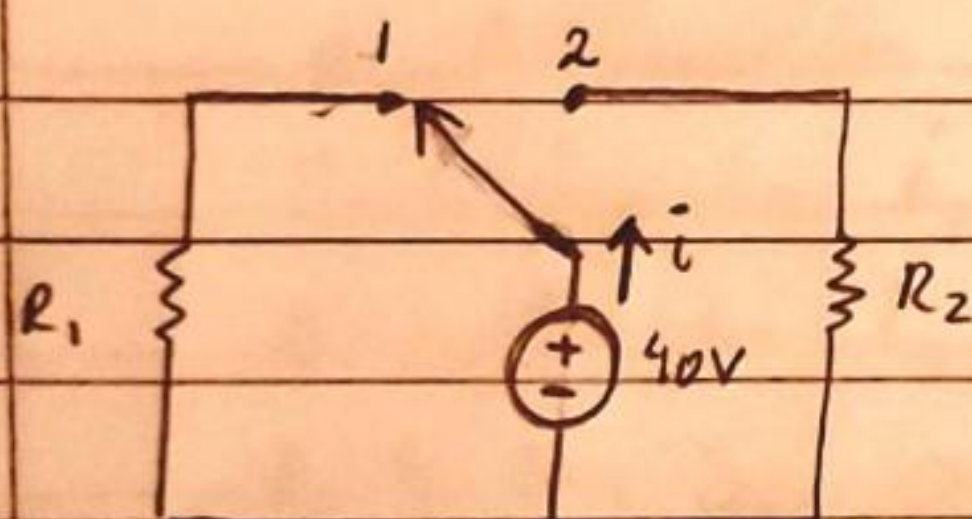B. Given the circuit below, and  $R_1 = 150 \Omega$  and  $R_2 = 330 \Omega$



- Calculate current  $i$  as switch is in position 1

↳ Apply ohm's law,  $V = R \cdot I$

$$\rightarrow I_1 = \frac{V}{R_1}; R_1 = 150 \Omega \quad V = 40 \text{ V}$$

$$\rightarrow I_1 = \frac{40 \text{ V}}{150 \Omega} = .266 \text{ A} \Rightarrow 266 \text{ mA}$$


C. Repeat B, compute switch in position 2

↳ recall rearrange of ohm's law

$$\rightarrow I_2 = \frac{V}{R_2}; V = 40 \quad R_2 = 330 \Omega$$

$$\rightarrow \text{Thus, } \frac{40}{330 \Omega} = .122 \text{ A} = 122 \text{ mA}$$

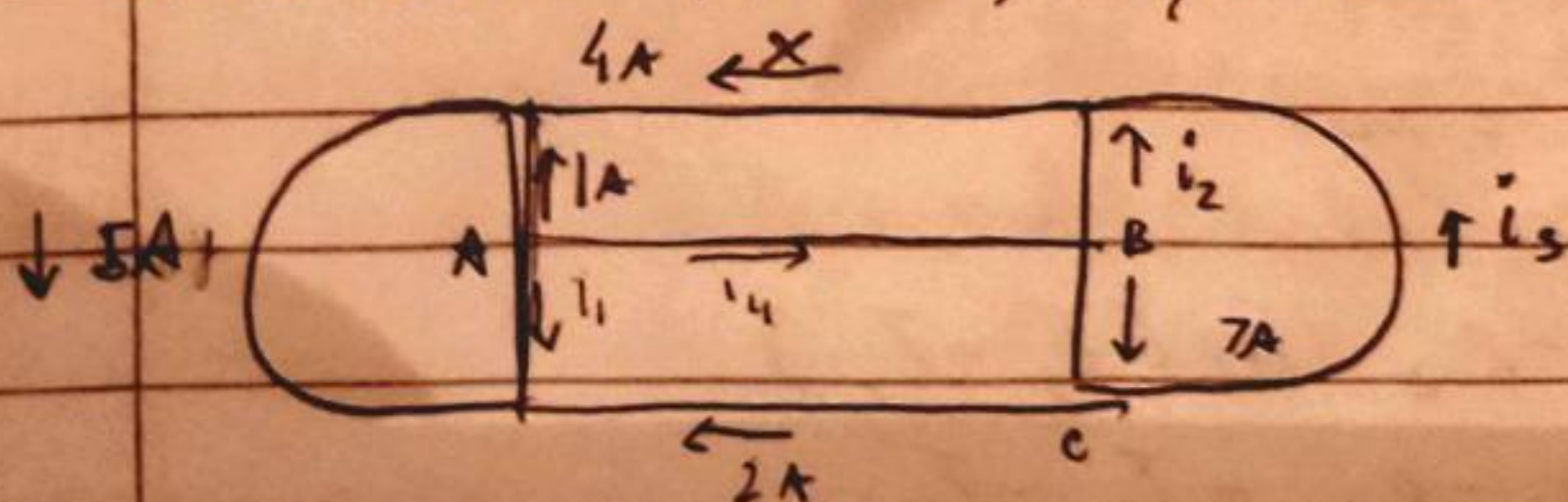2. Determine  $i_1, i_2, i_3, i_4$ , and consider  $x = 4 \text{ A}$  and  $y = 5 \text{ A}$



$$i_1 \rightarrow \text{Consider } \downarrow 5 \text{ A } \downarrow i_1 \leftarrow 2 \text{ A} \Rightarrow -i_1 - 5 \text{ A} - 2 \text{ A} = 0$$

$$\rightarrow -i_1 - 7 \text{ A} = 0; i_1 = -7 \text{ A} \checkmark$$

$$i_4 \rightarrow \text{Consider } \uparrow 1 \text{ A} \rightarrow i_4 \downarrow i_1 = -7 \text{ A}$$

$$\rightarrow 1 + i_4 - 7 = 0 \Rightarrow i_4 = 6 \text{ A} \checkmark$$

$$i_3 \rightarrow -7 \text{ A} + 2 \text{ A} + i_3 = 0 \Rightarrow i_3 = 5 \text{ V}$$

$$i_2 \rightarrow -i_2 - i_3 + 5 = 0$$

$$\rightarrow i_2 = 5 + 5 = 0$$

$$\rightarrow i_2 = 0$$


$$\text{Thus, } i_1 = -7 \text{ A}, i_2 = 0 \text{ A}, i_3 = 5 \text{ A}, i_4 = 6 \text{ A} \checkmark \text{ Page}$$



### Problem 2

B. Calc the  $V_1$  and  $V_2$  of the circuit below, given that

$$A = 19V, B = 11V, C = 10V$$

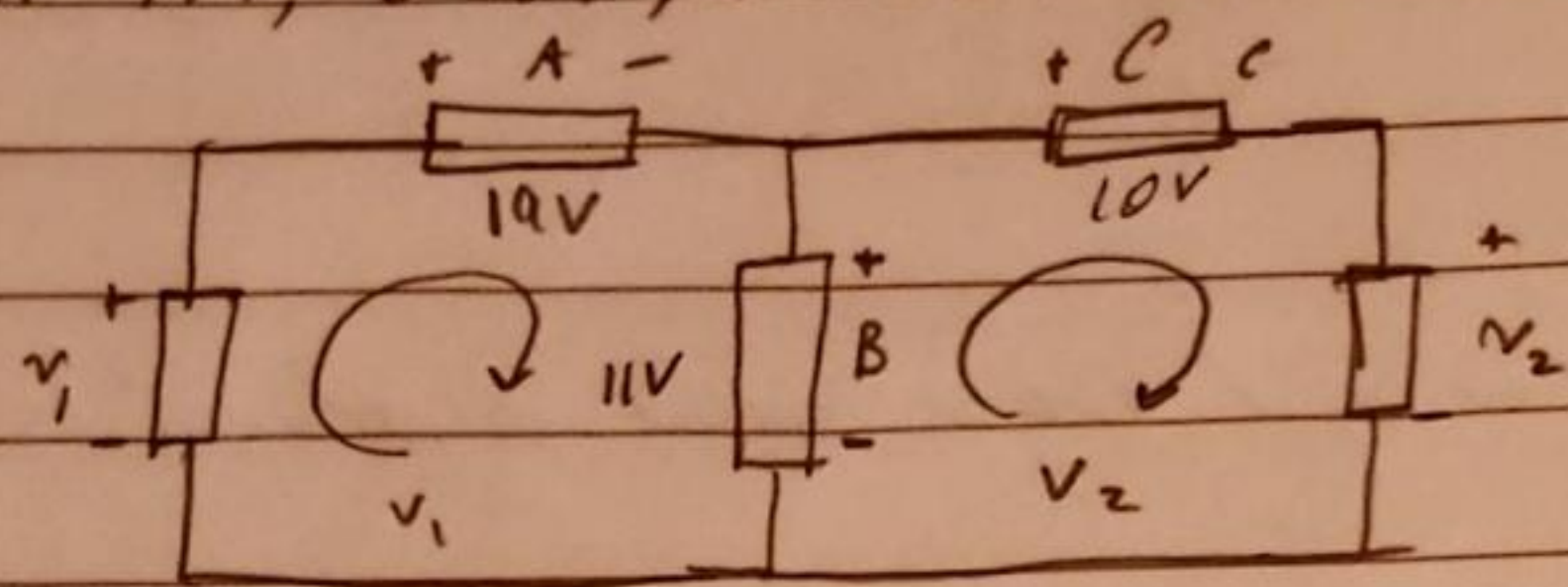

$$V_1 \rightarrow \text{Consider KVL} = V_1 - 19 + 11$$

$$\rightarrow V_1 - 19 - 11 = 0$$

$$\rightarrow V_1 = 30V \checkmark$$

$$V_2 \rightarrow \text{Consider one more KVL} = V_2 - 11 + 10$$

$$\rightarrow V_2 - 11 + 10 = 0$$

$$V_2 = 1V \checkmark$$

### Problem 3

Consider the fact that there is a linear relationship between the resistance and temperature of a semiconductor. Given that at  $25^\circ\text{C}$  the ohm resistance is  $5\Omega$ , and at  $100^\circ\text{C}$  there is  $340\Omega$ . Calculate the temperature at  $1k\Omega$  ( $\cdot 10^{-3}$ )

$$A \rightarrow \text{Consider } R_1 = 5000\Omega, T = 25^\circ\text{C}$$

$$R_2 = 340\Omega, T = 100^\circ\text{C}$$

B.  $\rightarrow$  Since there is a linear relationship, we can find slope

$$\rightarrow \frac{R_2 - R_1}{T_2 - T_1} = \frac{340 - 5000}{100 - 25} = -62.1 \Omega$$

$$C. \text{ Consider that } R_3 = 1k\Omega \Rightarrow 1000\Omega$$

$\rightarrow$  Similarly, slope between  $R_2$  &  $R_3$

$$\rightarrow \frac{R_3 - R_2}{T_3 - T_2} = m$$

$$\rightarrow R_3 - R_2 = m(T_3 - T_2)$$

$$\rightarrow \frac{R_3 - R_2}{m} = T_3 - T_2$$


$$\rightarrow \frac{R_3 - R_2}{m} - T_2 = T_3; T_2 = 100, T_3 = ? R_3 = 1000, R_2 = 340\Omega$$

$$\rightarrow 100 + \frac{1000 - 340}{-62.1} = 89.4^\circ\text{C} \checkmark$$




# Problem 4.

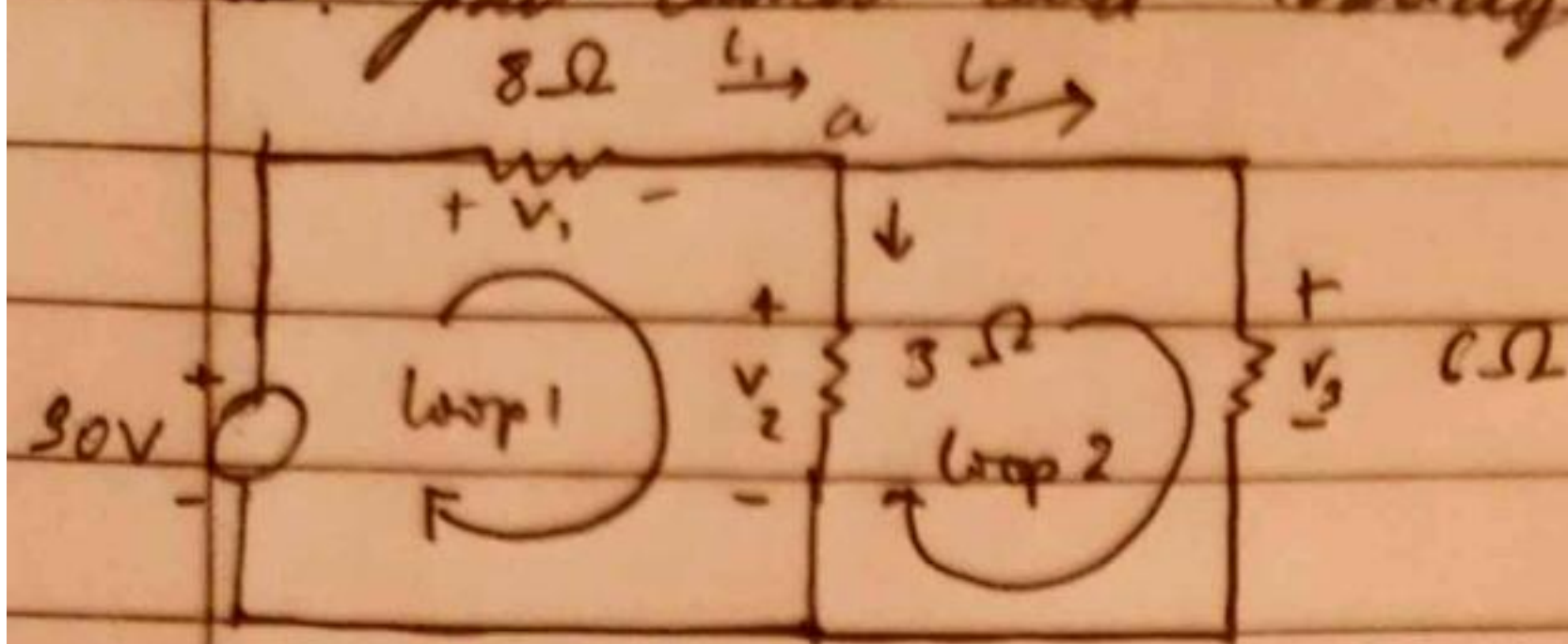a. Find current and voltage in the following circuit



↳ simplify the circuit

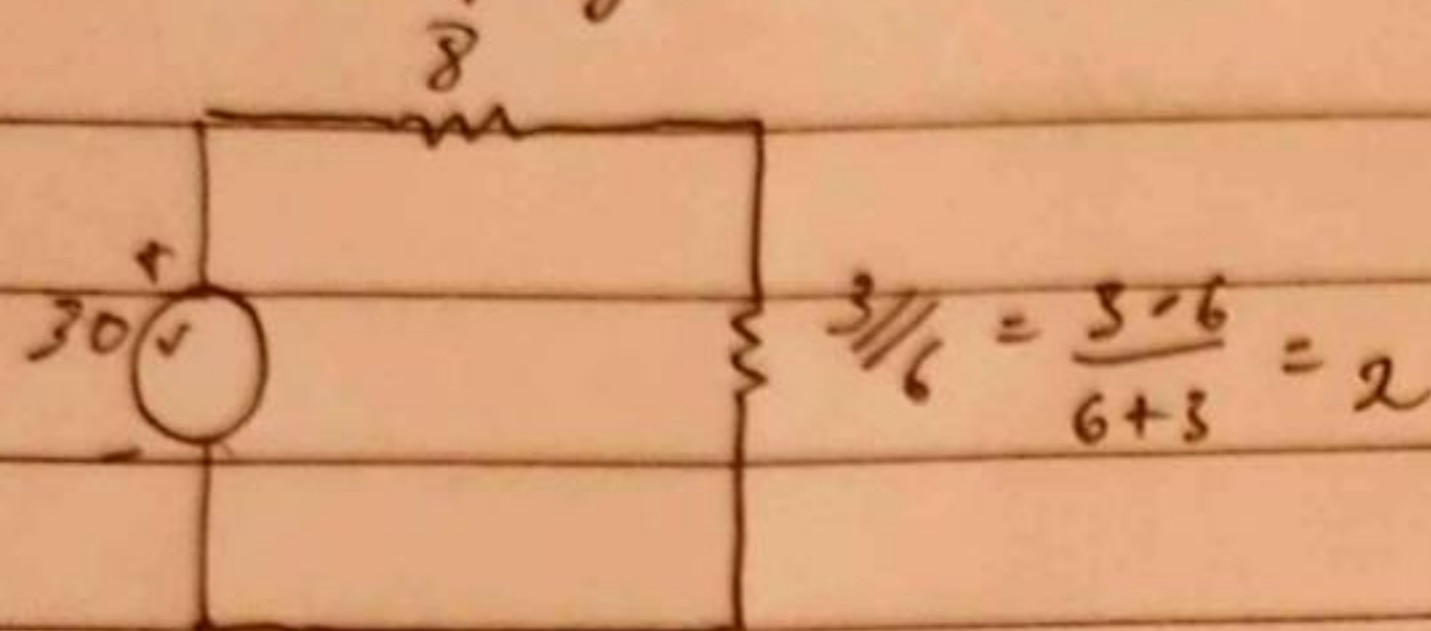

A. ↳ Consider  $R_{eq} = 8 + 2$  // series circuit

↳ Thus,  $R_{eq} = 10 \Omega$

B. ↳ Consider  $i_1 = \frac{V}{R_{eq}} = \frac{30}{10} = 3A \checkmark$

C. ↳ Consider  $i_2 = 3 \cdot \frac{6}{9} = 2A \checkmark$

D. ↳ Consider  $i_3 = 3 \cdot \frac{3}{9} = 1A \checkmark$

E. ↳ Consider  $v_1 = R \cdot I \Rightarrow 8 \cdot 3 \Rightarrow v_1 = 24V \checkmark$

F. ↳ Consider  $v_2 = R \cdot I \Rightarrow 3 \cdot 2 \Rightarrow 6V \checkmark$

G. ↳ Consider  $v_3 \Rightarrow 6 \cdot 1 = 6V \checkmark$

b. Compute power absorbed by each element

↳ Consider  $P = I^2 R$

↳ Thus,  $P_{8\Omega} = 3^2 \cdot 8 = 72W \checkmark$

$P_{3\Omega} = 2^2 \cdot 3 = 12W \checkmark$

$P_{6\Omega} = 1^2 \cdot 6 = 6W \checkmark$

c. Power supplied by each element

↳ Consider  $P = VI$


↳  $P_{30V} = 30 \cdot i_1 = 90W$ ;  $i_1 = 3 \checkmark$

↳  $P_{30V} = 30 \cdot i_2 = 60W$ ;  $i_2 = 2 \checkmark$

↳  $P_{30V} = 30 \cdot i_3 = 30W$ ;  $i_3 = 1 \checkmark$



# Problem 5

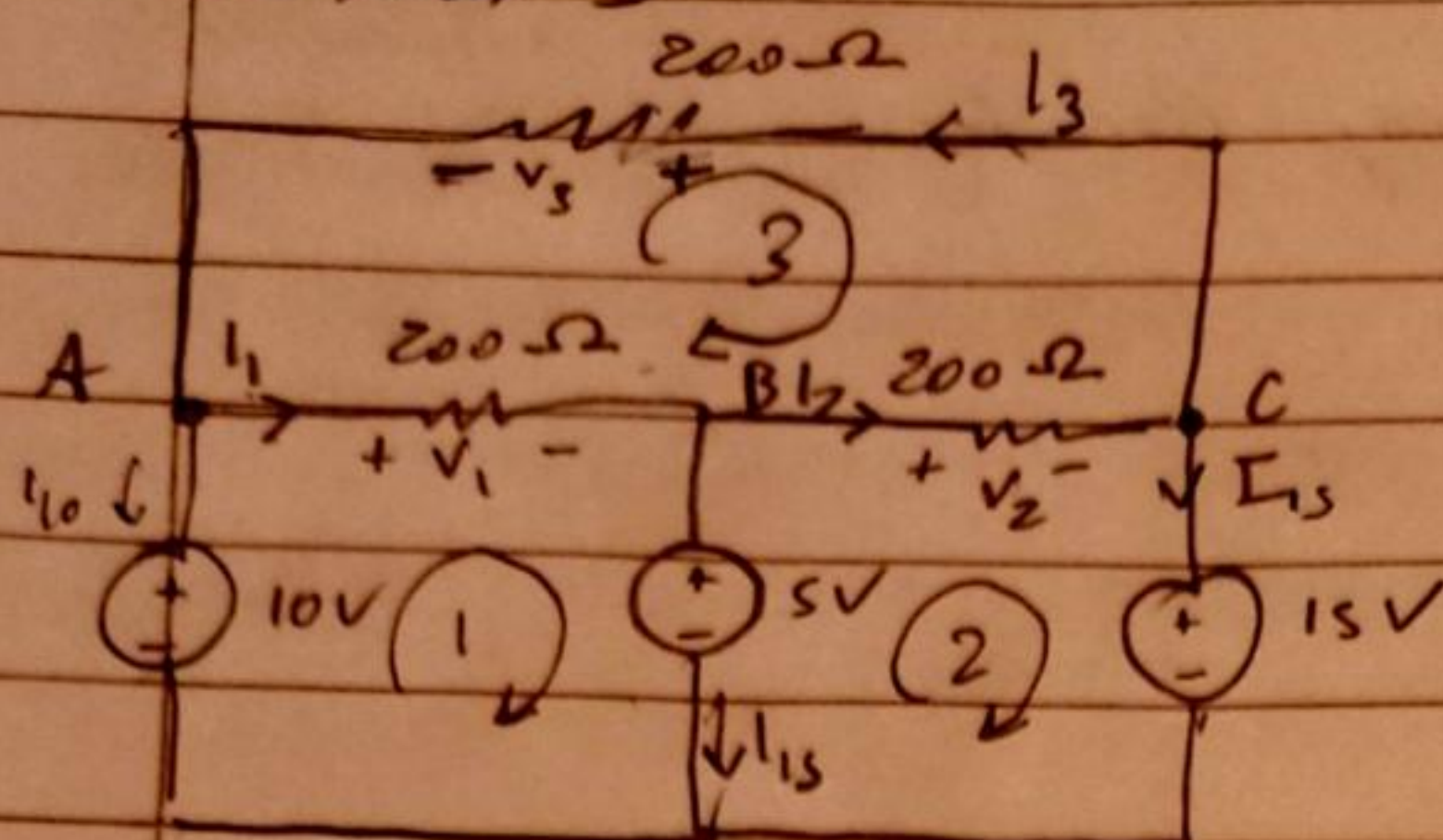

a. use KVL find voltage across each resistor

$$\hookrightarrow \text{KVL Loop}_1 = -10V + V_1 - 5 = 0$$

$$\hookrightarrow V_1 = 15V \checkmark$$

$$\hookrightarrow \text{KVL Loop}_2 = 5V + 15V + V_2 = 0$$

$$\hookrightarrow V_2 = -20V \checkmark$$

$$\hookrightarrow \text{KVL Loop}_3 = -15 - V_3 - (-20) = 0$$

$$\hookrightarrow -V_3 = -5 ; V_3 = 5V \checkmark$$

b. find current running through each resistor

$\hookrightarrow$  Consider Ohm's law;  $V = IR \Rightarrow I = V/R$

$$\hookrightarrow I_1 = \frac{15V}{200\Omega} = 0.075A = 75mA \checkmark$$

$$\hookrightarrow I_2 = \frac{-20}{200} = -\frac{1}{10} = -1mA \checkmark$$

$$\hookrightarrow I_3 = \frac{5}{200} = \frac{1}{40} = 25mA \checkmark$$

c. find current through each voltage source

$\hookrightarrow$  refer to diagram above.

$$\hookrightarrow \text{At A} \Rightarrow I_3 = I_{10} + I_1$$

$$\hookrightarrow I_{10} = 25 - 75$$

$$\hookrightarrow I_{10} = 50 \cdot 10^{-3}mA \checkmark$$

$$\hookrightarrow \text{At B} \Rightarrow I_1 = I_2 + I_5$$

$$\hookrightarrow I_5 = 75mA - (-1mA)$$

$$\hookrightarrow I_5 = 76 \cdot 10^{-3}mA \checkmark$$

$$\hookrightarrow \text{At C} \Rightarrow I_2 = I_3 + I_{15}$$

$$\hookrightarrow I_{15} = -1mA - 25mA$$

$$\hookrightarrow I_{15} = -26 \cdot 10^{-3}mA \checkmark$$