

Laboratory 4

Series and Parallel Circuits and the Node Voltage Method

Objectives

Students will:

- Familiarize with breadboards by constructing more complex circuits
- Analyze series-connected and parallel-connected circuits
- Study and verify node-voltage methods

Equipment and Components


- 2x Digital multimeters
- 2x Power supplies
- 1 Breadboard
- Cables and connecting wires as needed
- Resistors: 100 Ω , 270 Ω , 470 Ω , 680 Ω , 1 k Ω , 2.2 k Ω , 3.3 k Ω , 5.6 k Ω , 10 k Ω , 100 k Ω , 4.7 M Ω , 10 M Ω .

Preliminary Work

- Read Section 2.5, 2.6, 3.1, 3.2, 3.2 of the textbook.
- **Fill out the tables (theoretical values) for the given circuits.** Clearly indicate units for your solutions. Show your results to your instructor before starting the lab.

Procedures

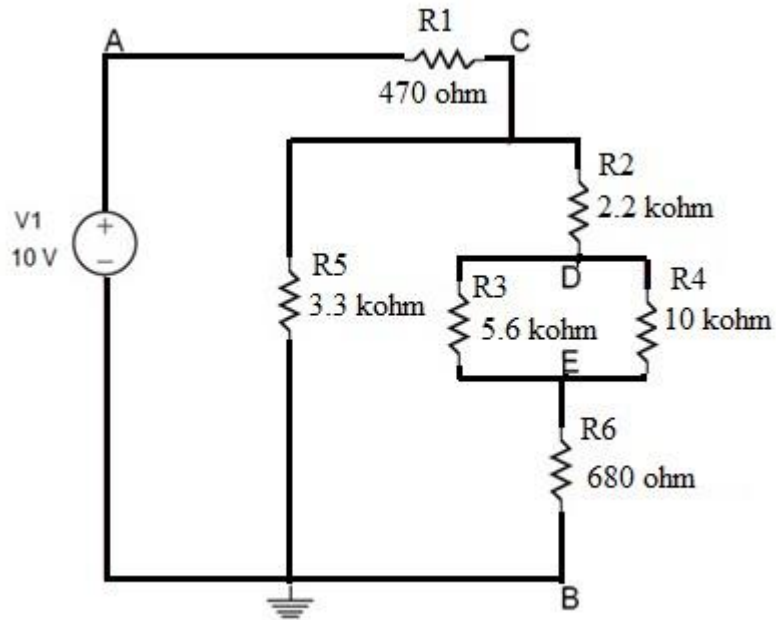1. A) construct the following circuit without the power supply on the breadboard.



- B) Measure the equivalent resistance seen by the source. What is the % error of the measured and calculated values of this equivalent resistance?

	Theoretical Value*	Measured Value	% Error
Equivalent resistance			

ENGR 065 Circuit Theory: Laboratory 4

2. Apply 10 V to the circuit and measure the following currents and voltages shown in the table below. **Note:**

- to measure V_{XY} , the red lead of the DMM (Digital Multimeter) should be at point X and the black lead at point Y of the circuit. For example, to measure V_{AC} , the red lead of the DMM should be at point A and the black lead at point C of the circuit
- to measure V_X , the red lead of the DMM should be at point X and the black lead at Ground (point B in the above circuit.)

Variable	Theoretical Value*	Measured Value
I_{R1}		
I_{R2}		
I_{R3}		
I_{R4}		
I_{R5}		
I_{R6}		

Variable	Theoretical Value*	Measured Value
V_A		
V_B		
V_C		
V_D		
V_E		

Variable	Theoretical Value*	Measured Value
V_{AC}		
V_{CD}		
V_{DE}		
V_{EB}		
V_{CE}		

ENGR 065 Circuit Theory: Laboratory 4

3. If R_1 is removed from the circuit, what would be the value of V_D ? Explain.

Variable	Theoretical Value*	Measured Value
V_D		


4. If R_6 is removed from the circuit, what would be the value of V_D ? Explain.

Variable	Theoretical Value*	Measured Value
V_D		

5. If R_5 is removed from the circuit, would the current in R_1 increase or decrease?

ENGR 065 Circuit Theory: Laboratory 4

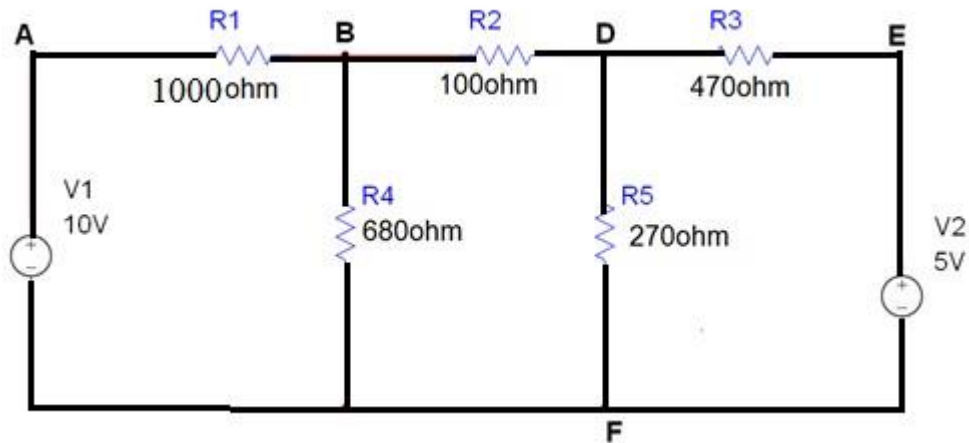6. Construct the circuit shown below on the breadboard. Use the DC power supply to provide the two voltage sources as shown in the circuit. **Node F is the reference node.**



7. Measure and fill out the voltages in the table below. Verify the KVL for each loop in the circuit.

Variable	Theoretical Value*	Measured Value
V_{AB}		
V_{BD}		
V_{DE}		
V_{EF}		
V_{AF}		
V_{BF}		
V_{DF}		

Questions and conclusions

- Summarize your findings and explanations in response to the questions posed in this lab.

Note: **Please, clean up and put everything in their original places before leaving labs!**