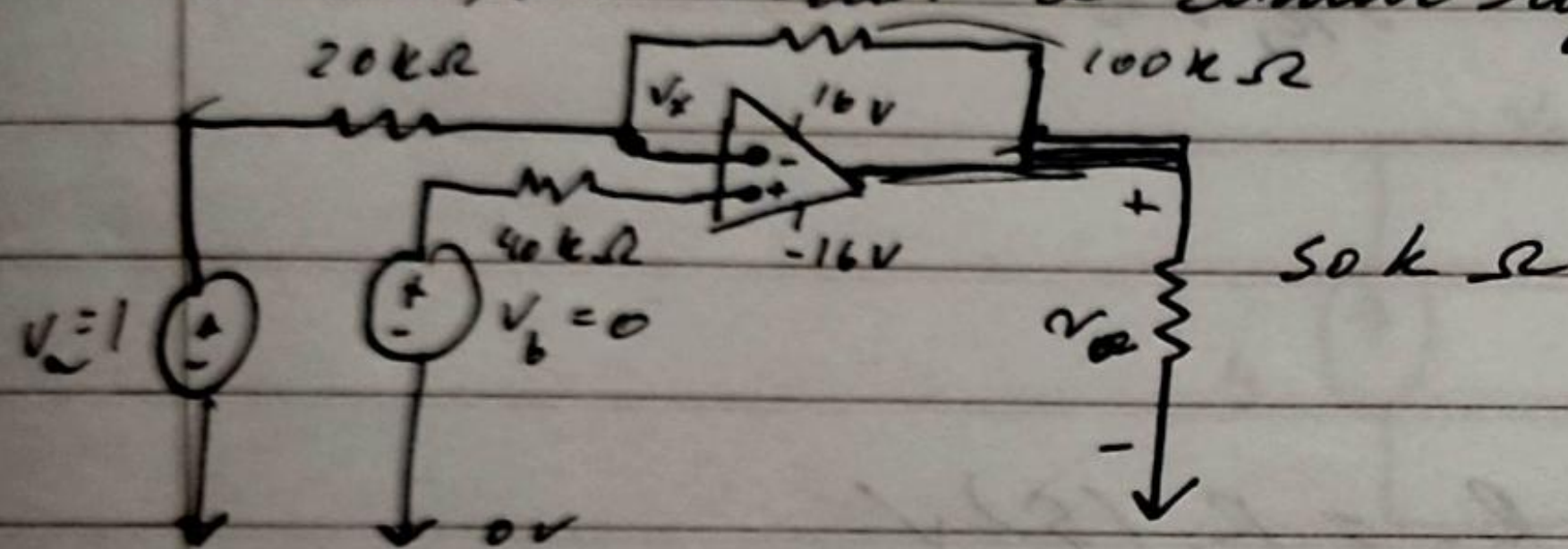


Engr 688

Homework 6

1. Consider Op amplifier, compute V_o given $V_a = 1V$, $V_b = 0V$; assume the circuit is in a linear region.




i. Consider $\frac{V_a - V_x}{1k} = \frac{V_x - V_o}{10k}$

ii. Consider linear circuit graph


$$\hookrightarrow \frac{1-0}{20} = \frac{0-V_o}{100}$$

$$\hookrightarrow \frac{1}{20} = \frac{V_o}{100}$$
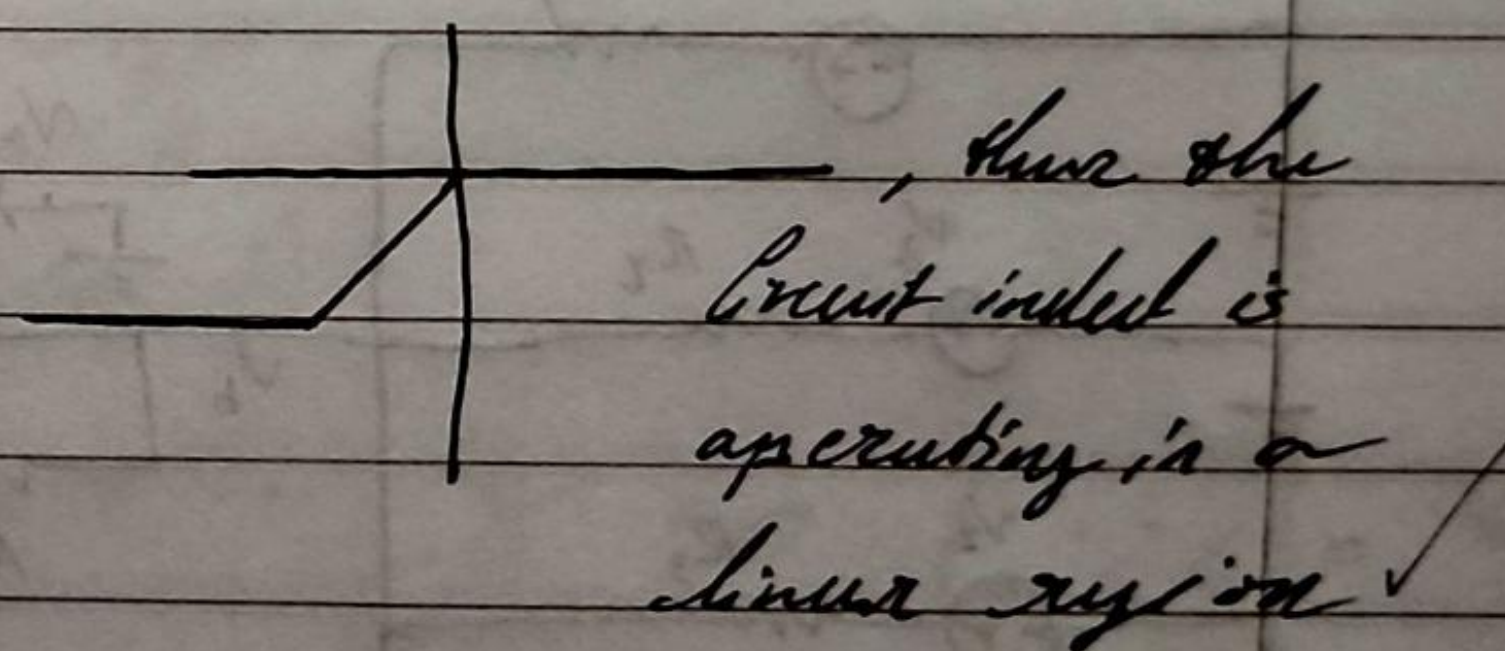
$$\hookrightarrow V_o = \frac{100}{20} = -5V \checkmark$$



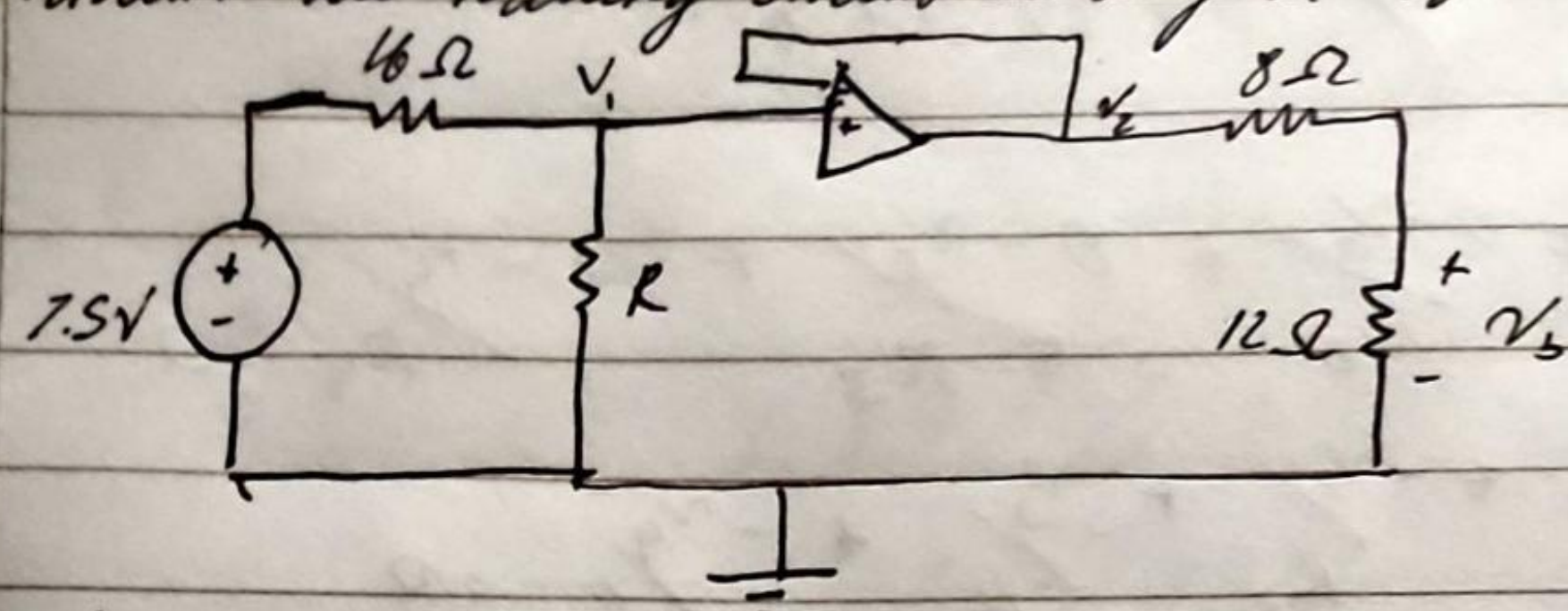2. Circuit the following circuit and find V_o .



i. Consider ideal op-amp properties

a. $V^+ = V^-$; $R = 29$

ii. Voltage Division from 7.5V

$$\hookrightarrow V_1 = \frac{R(7.5)}{R+16} = \frac{29(7.5)}{29+16} = 4.83V$$


iii. Voltage across V_2

$$\hookrightarrow V_o = V_2 = \frac{12}{12+8} V_1; \quad V_2 = V_1 = 4.83$$

$$\hookrightarrow V_o = 4.83 \left(\frac{12}{12+8} \right) = 2.89V$$

3. Select R_1 & R_2 such that

$$V_o = 6V_s$$

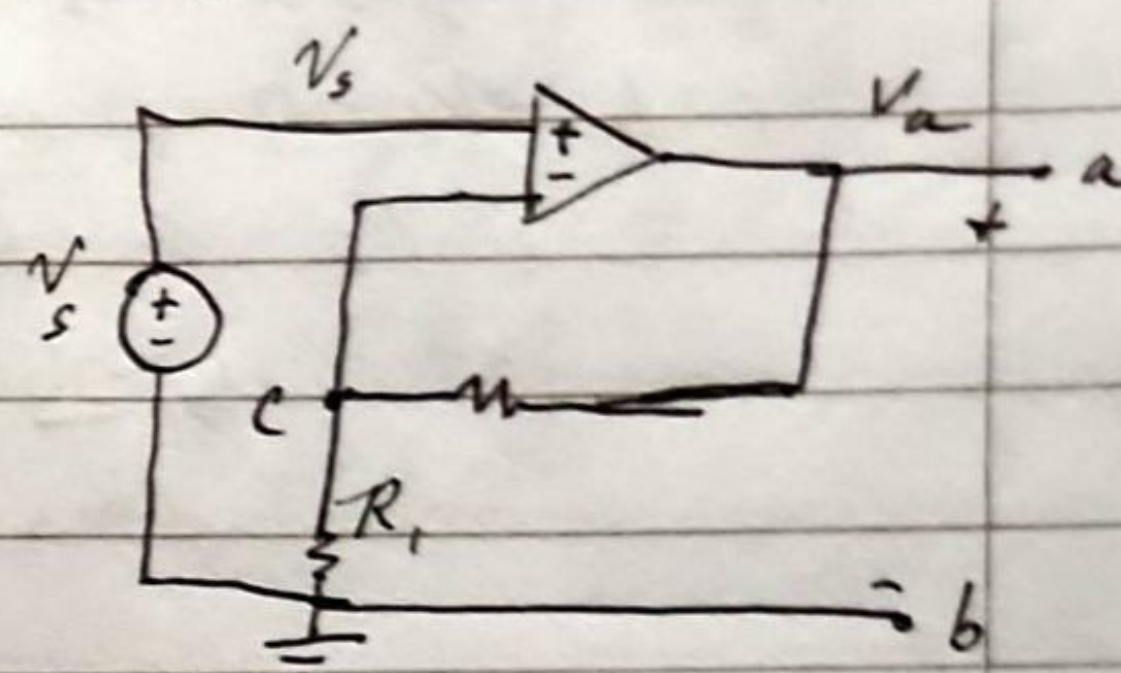

consider $V_s = V_o = V_1$

• KVL at node C

$$\frac{0 - V_c}{R_1} = \frac{V_c - V_o}{R_2}$$

$$\hookrightarrow \frac{V_c}{R_1} = \frac{V_c}{R_2} - \frac{V_o}{R_2}$$

$$\hookrightarrow \text{Then, } \frac{V_o}{R_2} = \frac{V_c}{R_2} + \frac{V_c}{R_1}$$

$$\hookrightarrow \left(V_c \left(\frac{R_1 + R_2}{R_1 R_2} \right) \right) = \frac{V_o}{R_2}$$

$$\hookrightarrow V_o = V_c \left(\frac{R_1 + R_2}{R_1} \right)$$

$$\hookrightarrow V_o = V_c \left(1 + \frac{R_2}{R_1} \right)$$

i. Optimal ideal law

$$\hookrightarrow V_c = V_s; \quad V_o = V_s \left(1 + \frac{R_2}{R_1} \right) \rightarrow$$

3. Continued...

↳ Recall $V_a = V_s (1 + R_2/R_1)$

iii. Consider $V_0 = V_a - V_b = V_s (1 + R_2/R_1) - 0$

↳ $V_0 = (1 + R_2/R_1) V_s$; $V_s = 6$


↳ Therefore, $6 V_s = (1 + R_2/R_1) V_s =$

iv. Therefore, $6 = 1 + R_2/R_1$

↳ $R_2/R_1 = 5$ ✓

v. Now Consider $R_2/R_1 = 5 \Rightarrow R_2 = R_1 (5)$ ✓

4. Consider the Circuit

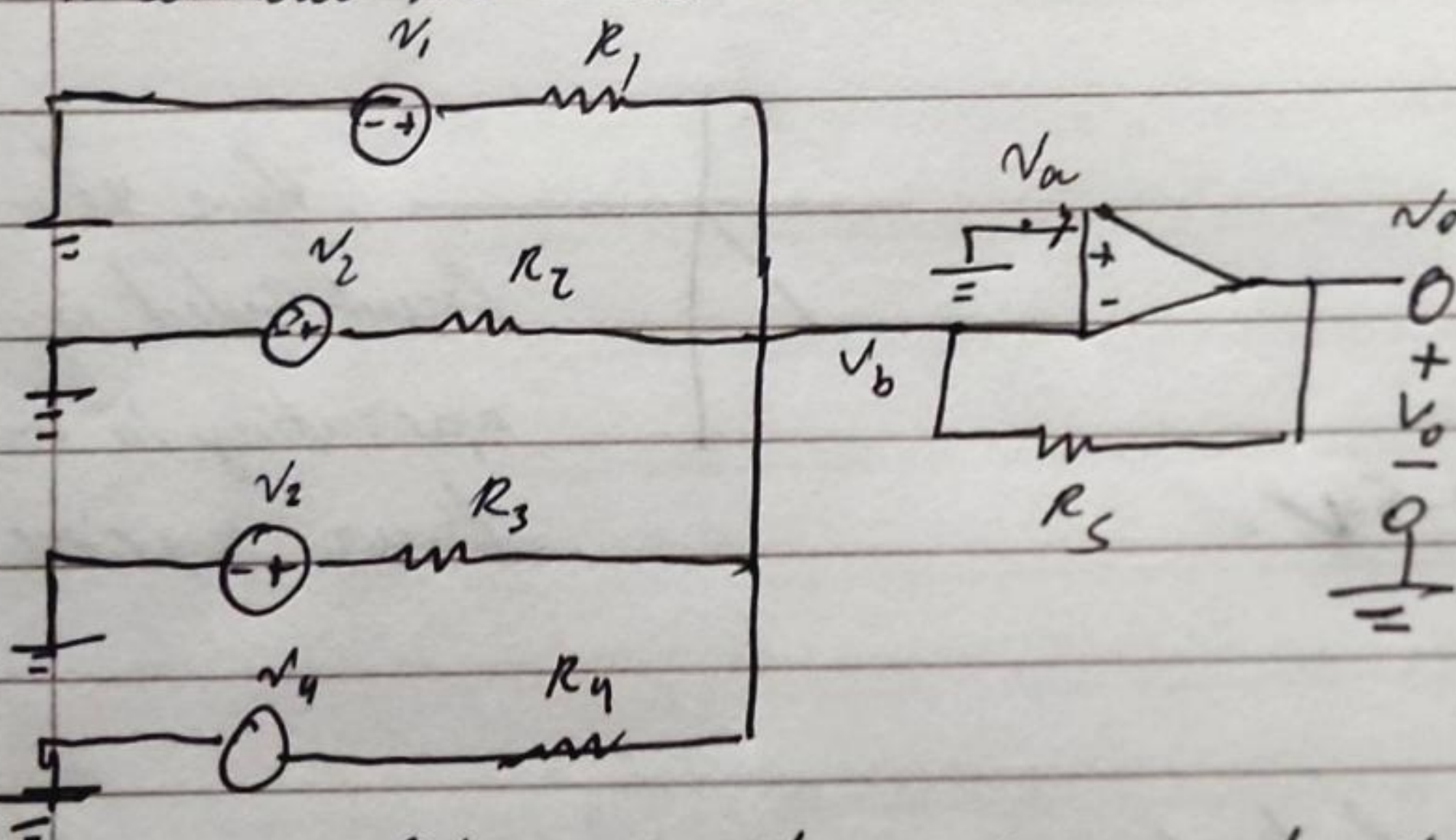

a. Determine V_0 in terms of V_1, V_2, V_3, V_4 .

↳ Node Analysis at V_b

$$\frac{V_0 - 0}{R_S} + \frac{0 - V_1}{R_1} + \frac{0 - V_2}{R_2} + \frac{0 - V_3}{R_3} + \frac{0 - V_4}{R_4} = 0$$

$$\frac{V_0}{R_S} + \frac{-V_1}{R_1} + \frac{-V_2}{R_2} + \frac{-V_3}{R_3} + \frac{-V_4}{R_4} = 0$$

$$\frac{V_0}{R_S} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4}$$

$$\text{Thus, } V_0 = -R_S \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right)$$

b. Consider $R_S = 1k\Omega$, then


↳ Given $V_0 = -1/4 (V_1 + V_2 + V_3 + V_4)$

↳ substitution $\Rightarrow -1/4 (V_1 + V_2 + V_3 + V_4) = -1k \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right)$

↳ Thus, $R_1 = 4k, R_2 = 4k, R_3 = 4k, R_4 = 4k$

Problem No. 3

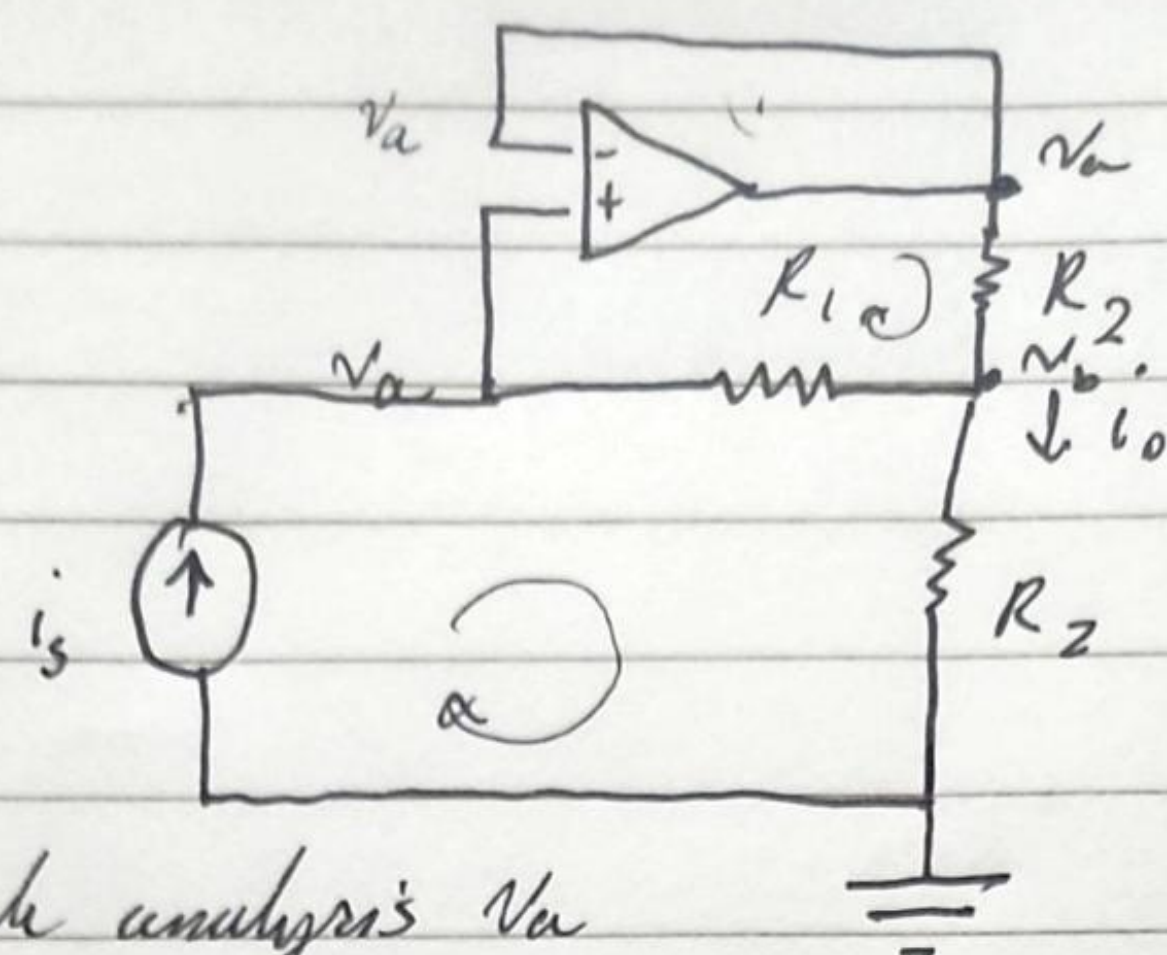a. Consider the non-inverting current, show $i_o = k i_s$ where k is the current gain.



↳ Node analysis V_a

$$a. \rightarrow \frac{V_a - V_b}{R_1} - i_s = 0$$

$$\rightarrow i_s = \frac{V_a - V_b}{R_1}$$

b. Node Equation for Node b

$$\frac{V_b - V_a}{R_2} + \frac{V_b}{R_2} + \frac{V_b - V_a}{R_1} = 0 \quad \left[\because i_s = \frac{V_a - V_b}{R_1} \right]$$

$$\rightarrow \frac{V_b - V_a}{R_2} + i_o - i_s = 0 \quad \left[\because -i_s = \frac{V_b - V_a}{R_1} \right]$$

$$\rightarrow -\frac{R_1 i_s}{R_2} + i_o - i_s = 0 \quad \left[\because V_b - V_a = -R_1 i_s \right]$$

$$\rightarrow i_o = i_s \left[\frac{R_1}{R_2} + 1 \right]$$

$$\rightarrow \text{Hence, } k = \frac{R_1}{R_2} + 1 \quad \checkmark$$

$$b. k = \frac{R_1}{R_2} + 1 ; \text{ Consider } R_1 = 11 \text{ k}\Omega$$

$$\rightarrow \frac{11 \text{ k}\Omega}{1 \text{ k}\Omega} + 1$$

$$R_2 = 1 \text{ k}\Omega$$

$$\rightarrow k = 12 \quad \checkmark$$